

Electrical Engineering

Prepared by

Dr. Abduljabbar H. Hammadi
Ph.D. Power Engineering

Chapter - 1 - Introduction

1.1 - SI Units

International system of unit
(SI) or (m. kg. s)

<u>Quantity</u>	<u>Unit</u>	<u>Unit Symbol</u>
Length	metre	m
Mass	Kilogram	kg
Time	Second	s
Electric current	Ampere	A (amp.)
Temperature	Kelvin	K
Illumination intensity	Candela (candle)	cd
Substance	Mole	Mol

1.2 - Ohm's Law

The ratio of potential difference (V) between any two points on a conductor to the current (I) flowing between them, is constant, provided the temperature of conductor does not change.

$$\frac{V}{I} = \text{constant} \quad \text{or} \quad \frac{V}{I} = R \quad \text{--- (1.1)}$$

Where

V : applied voltage (Volt).


I : Current (A)

R : Resistance (ohm) or (Ω)

-4-

The resistance can be defined from the dimension, length (l) and area (A)

$$R \propto \frac{l}{A}$$

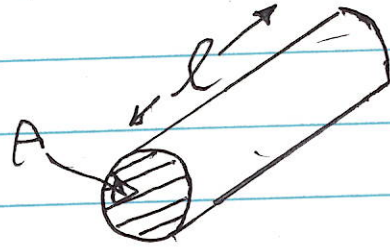

$$R = \rho \frac{l}{A} \quad \text{--- (1.2)}$$

Where ρ is the resistivity ($\Omega \cdot m$)

For Copper $\rho = 1.72 \times 10^{-8} (\Omega \cdot m)$ at $20^\circ C$

For Rubber $\rho = 10^{10} (\Omega \cdot m)$

The reciprocal of resistance (R) is the conductance (G) (mho or Ω^{-1})

$$G = \frac{1}{R} \quad \text{--- (1.3)}$$

From eqn. (1.2)

$$G = \frac{1}{\rho \frac{l}{A}} = \frac{1}{\rho} \cdot \frac{A}{l} = \sigma \frac{A}{l} \quad \text{--- (1.4)}$$

σ is the conductivity (Siemens / metre)


1.3 - Resistances Connection

a - Resistance in Series

$$V = V_1 + V_2 + V_3$$

$$I R_{eq} = I R_1 + I R_2 + I R_3$$
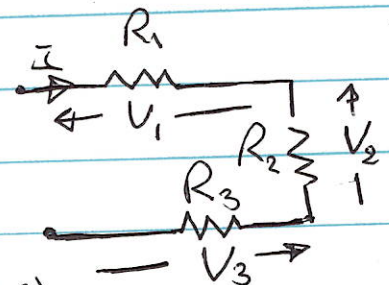
$$R_{eq} = R_1 + R_2 + R_3 \quad \text{--- (1.5)}$$




Where R_{eq} is equivalent resistance

b. Resistance in parallel

$$I = I_1 + I_2 + I_3$$

$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$
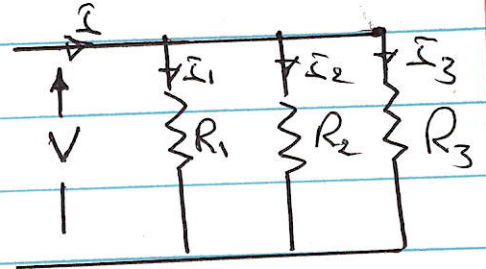
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \quad \text{--- (1.6)}$$



c. Combined Connection



$$R^- = R_2 // R_3$$

$$\frac{1}{R^-} = \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R^-} = \frac{R_2 + R_3}{R_2 R_3}$$


$$\therefore R^- = \frac{R_2 R_3}{R_2 + R_3}$$

$$\therefore R_{eq} = R_1 + R^- + R_4$$

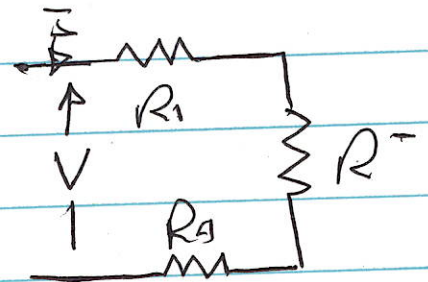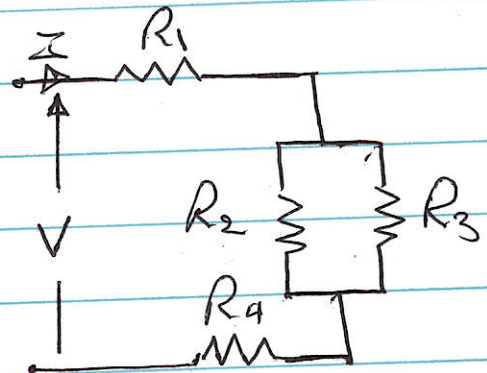

Ex (1.1): Calculate the total current for the circuit shown in Fig.

$$R^- = 4 + 2 = 6 \Omega$$

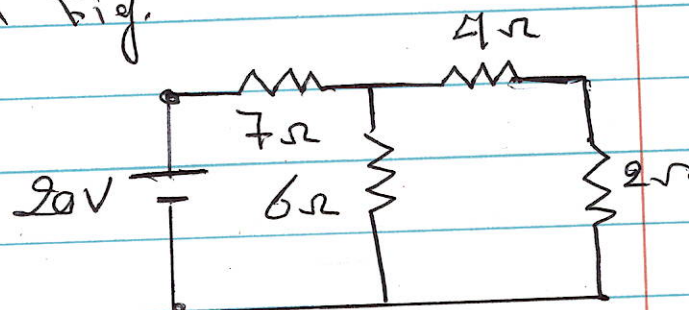

I.

DC

b - Current divider

$$R^- = R_1 \parallel R_2$$

$$I = I_1 + I_2$$

$$\frac{V^-}{R^-} = \frac{V^-}{R_1} + \frac{V^-}{R_2}$$

$$\frac{1}{R^-} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 R_2}$$

$$\therefore R^- = \frac{R_1 R_2}{R_1 + R_2}$$

$$I_1 = \frac{V^-}{R_1}$$



$$\therefore V^- = I_1 R_1$$

$$I R^- = I_1 R_1$$

$$I \cdot \frac{R_1 R_2}{R_1 + R_2} = I_1 R_1$$

$$\therefore I_1 = I \frac{R_2}{R_1 + R_2} \quad (A) \quad \dots (1.8)$$

1.5 - Star - Delta Transformation

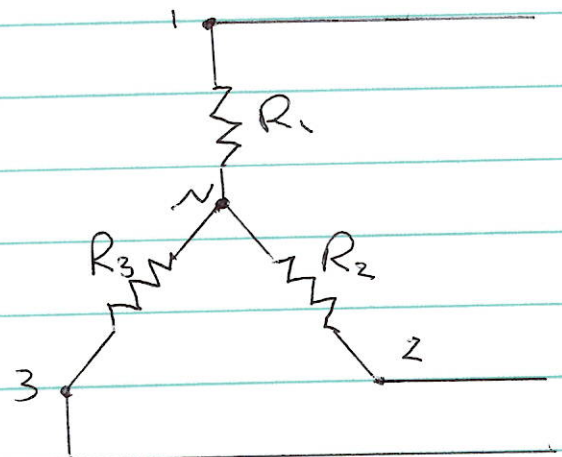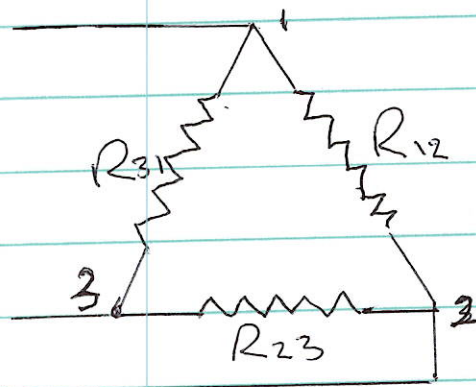

$$R_{12} = R_1 + R_2 + \frac{-8-}{R_3}$$

$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$

$$R_{31} = R_1 + R_3 + \frac{R_1 R_3}{R_2}$$

--- (1.10)


Q(1.2): Find the equivalent resistance of the network show in Fig. An ~~resistor~~

$$R_{1N} = \frac{6 \times 9}{6 + 9 + 2} = \frac{24}{12} = 2$$

$$R_{2N} = \frac{6 \times 2}{6 + 9 + 2} = \frac{12}{12} = 1$$




$$R_{3N} = \frac{9 \times 2}{6 + 9 + 2} = \frac{8}{12} = 0.666$$
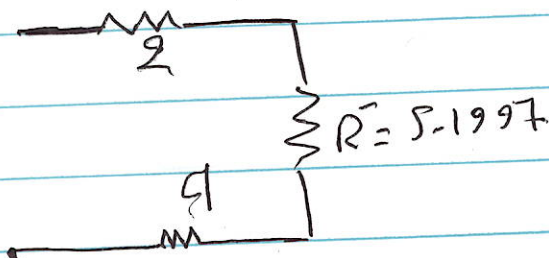
$$R' = \frac{8.666 + 13}{8.666 + 13} = 5.1997$$




$$R_{eq} = R_{AB} = 2 + 5.1997 + 4 = 11.1997 \Omega$$

equivalent resistance

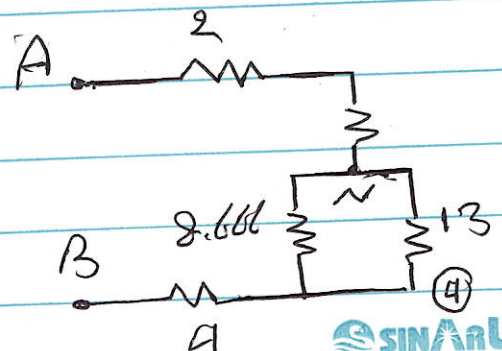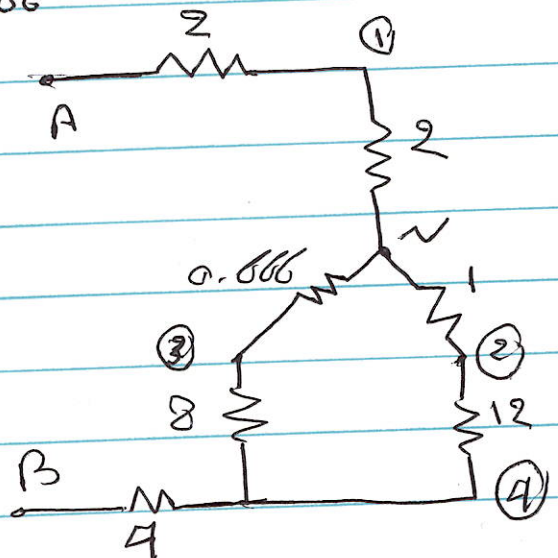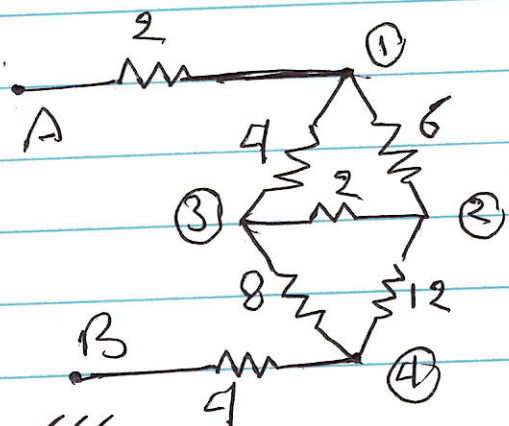

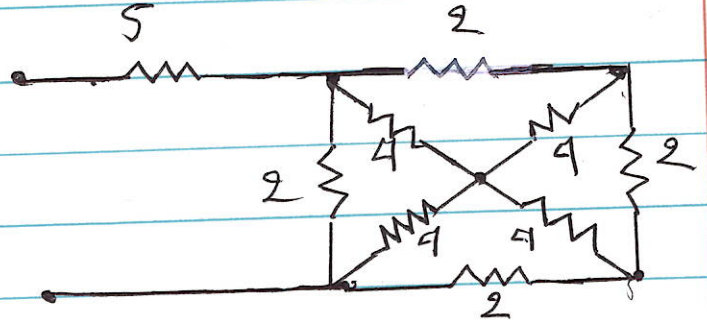Ex(1.3): Use Δ -Y conversion to find resistance between A and B. All resistances in Ohm
(Ans. $R_{AB} = 6.249 \Omega$)



1.6 - Power in DC Circuit

$$P = V \cdot I \quad \text{--- (1.11)}$$

$$V = IR$$

$$P = I^2 R \quad \text{--- (1.12)}$$

$$P = \frac{V^2}{R} \quad \text{--- (1.13)}$$

Chapter - 2 -

DC Circuits Theorems


2.1 - Kirchhoff's Laws

a - Kirchhoff's Current Law (KCL)


The algebraic sum of currents at node equal to zero.

b - Kirchhoff's Voltage Law (KVL)

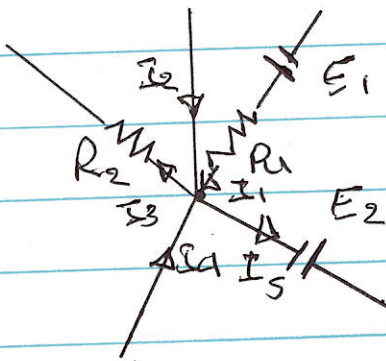The algebraic sum of voltages in closed loop (circuit) equal to algebraic sum of emf's.



KCL

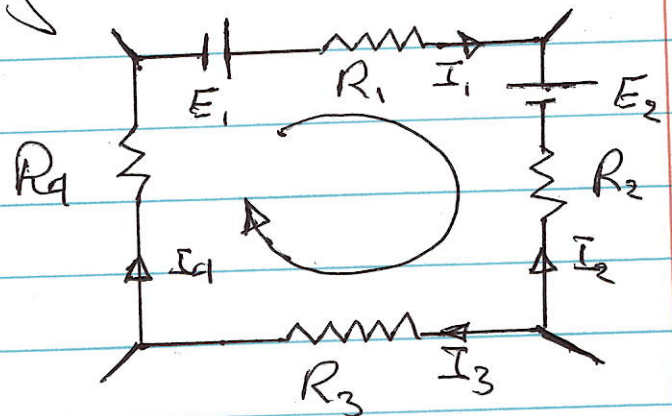

KVL

2.2 - Maxwell's Loops Method (mesh method)

$$\text{Loops} = b + 1 - j$$

b: branches


j: nodes

$$\text{Loops} = 5 + 1 - 3 = 3$$

KVL for loop (1)



$$R_1 I_1 + R_4 (I_1 - I_2) = E_1 - E_2$$
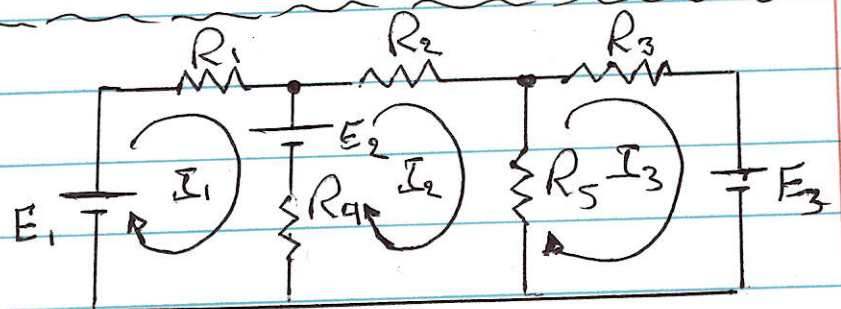
$$(R_1 + R_4) I_1 + R_4 I_2 + 0 I_3 = E_1 - E_2$$



EX(2.1)

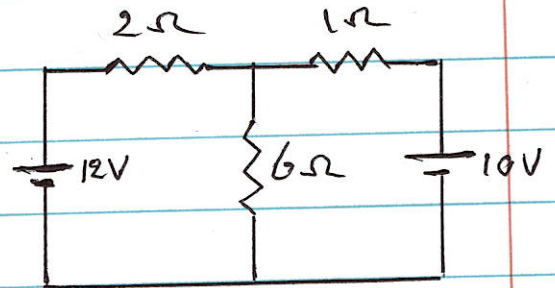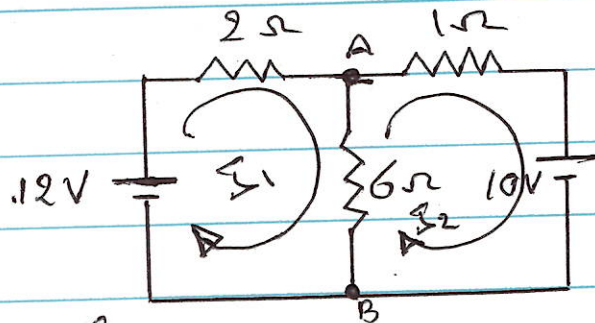Using maxwell's loops method find current in 6Ω resistance.



$$\text{loops} = 3 + 1 - 2 = 2$$

loop ①

$$(2+6)I_1 - 6I_2 = 12$$

$$8I_1 - 6I_2 = 12$$

loop ②

$$(1+6)I_2 - 6I_1 = -10$$

$$-6I_1 + 7I_2 = -10$$

$$\begin{bmatrix} 8 & -6 \\ -6 & 7 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 12 \\ -10 \end{bmatrix}$$

$$\Delta = \det \begin{bmatrix} 8 & -6 \\ -6 & 7 \end{bmatrix} = 8 \times 7 - (-6)(-6) = 56 - 36 = 20$$

$$\Delta_1 = \begin{bmatrix} 12 & -6 \\ -10 & 7 \end{bmatrix} = 12 \times 7 - (-10)(-6) = 84 - 60 = 24$$


$$\Delta_2 = \begin{bmatrix} 8 & 12 \\ -6 & -10 \end{bmatrix} = 8(-10) - (-6)(12) = -80 + 72 = -8$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{24}{20} = 1.2 \text{ amp} \quad I_2 = \frac{\Delta_2}{\Delta} = \frac{-8}{20} = -0.4$$


$$I_{6\Omega} = I_1 - I_2 = 1.2 - (-0.4) = 1.6 \text{ amp} \quad \text{From A to B}$$

Ex(2.2)

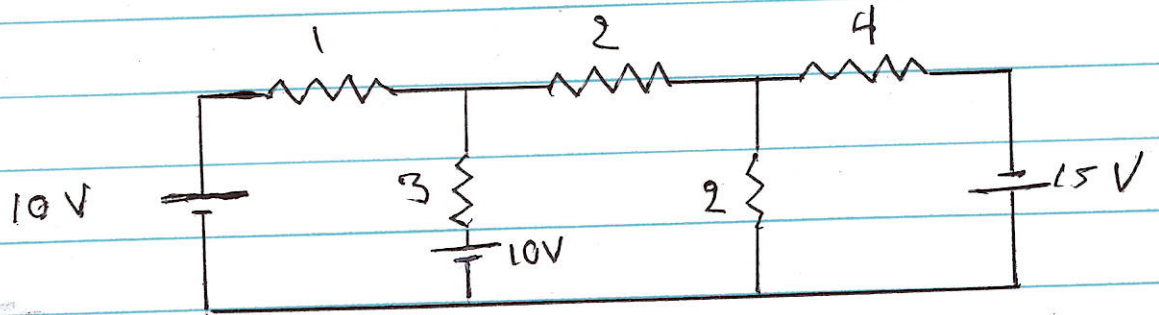Using Maxwell's loops method, find current in the 3Ω resistance.



Solution

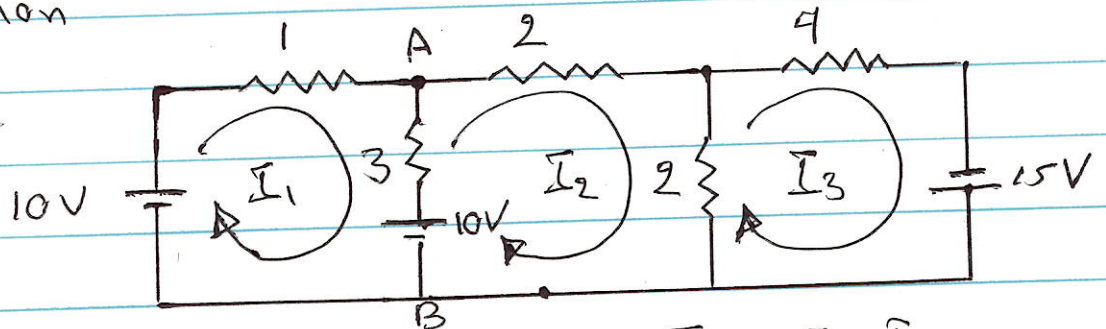

$$\text{Loops} = b + 1 - j = 5 + 1 - 3 = 3$$

$$I_{3A} = I_1 - I_2$$

loop ①

$$(1+3)I_1 - 3I_2 = 10 - 10$$

$$4I_1 - 3I_2 + 0I_3 = 0$$

loop ②

$$(2+2+3)I_2 - 3I_1 - 2I_3 = 10$$

$$-3I_1 + 7I_2 - 2I_3 = 10$$

loop ③

$$(4+2)I_3 - 2I_2 = 15$$

$$0I_1 - 2I_2 + 6I_3 = 15$$

$$\begin{bmatrix} 4 & -3 & 0 \\ -3 & 7 & -2 \\ 0 & -2 & 6 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 10 \\ 15 \end{bmatrix}$$

$$\Delta = \det \begin{bmatrix} 4 & -3 & 0 \\ -3 & 7 & -2 \\ 0 & -2 & 6 \end{bmatrix} = 4(7 \times 6 - (-2)(-2)) - (-3)((-3)6 - 0 \times (-2)) + 0((-3)(-2) - (6)(7)) = 98$$

-14-

$$\Delta_1 = \begin{bmatrix} 0 & -3 & 0 \\ 10 & 7 & -2 \\ 15 & -2 & 6 \end{bmatrix} = 0(7 \times 6 - (-2)(-2)) - (-3)(10 \times 6 - (-2)(15)) \\ = 270$$

$$\Delta_2 = \begin{bmatrix} 4 & 0 & 0 \\ -3 & 10 & -2 \\ 0 & 15 & 6 \end{bmatrix} = 4(10 \times 6 - (-2)(15)) : 0 + 0 = 360$$


$$I_1 = \frac{\Delta_1}{\Delta} = \frac{270}{98} = 2.755 \text{ amp.}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{360}{98} = 3.673 \text{ amp.}$$

$$I_{3\Omega} = I_2 - I_1 = 3.673 - 2.755 = 0.918 \text{ amp From B to A}$$


Q-1 Using maxwell's loops method, find current in the 8Ω resistance

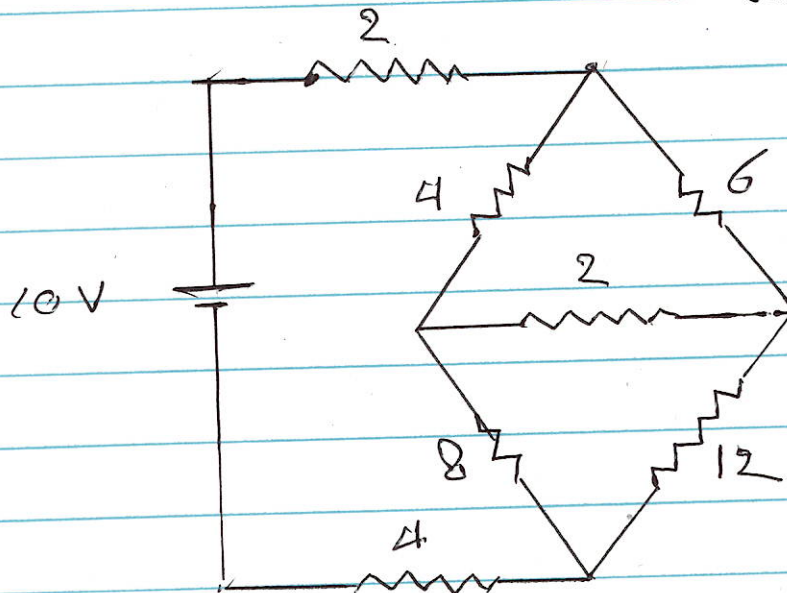(Ans: $I_{8\Omega} = 0.4545 \text{ amp.}$)




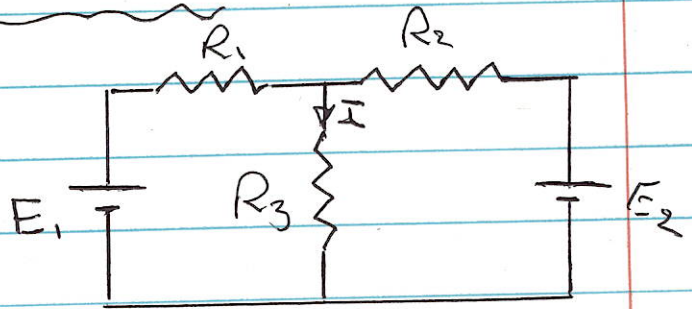2.3 - Superposition Theorem


Assume we have the circuit shown, and we want to calculate the current in R_3 (I)



1 - Current from source E_1 , I'

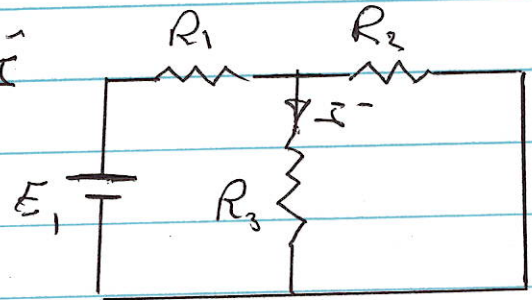


2 - Current from source E_2 , I''

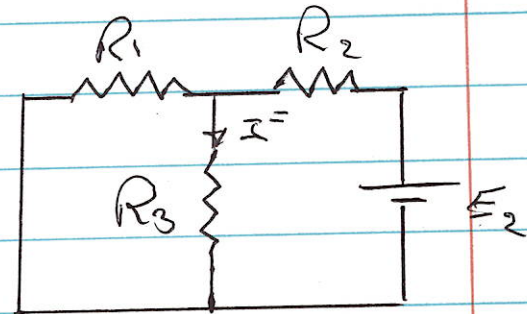

$$\therefore I = I' + I''$$

Ex(2.3)

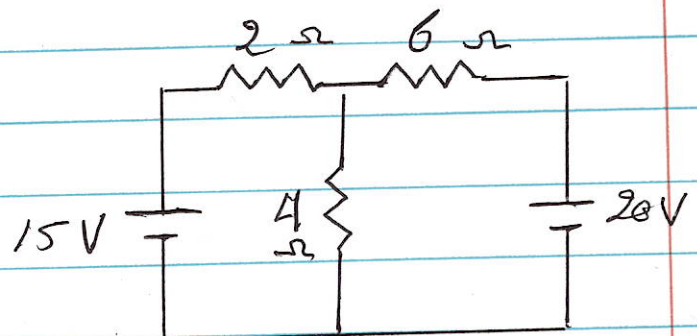
Using superposition theorem find current in 4Ω resistance



1 - Current from source 15V, I'


$$I' = \frac{15}{2+2.4} = 3.0109 \text{ amp.}$$

$$I'' = I' \cdot \frac{6}{6+4}$$

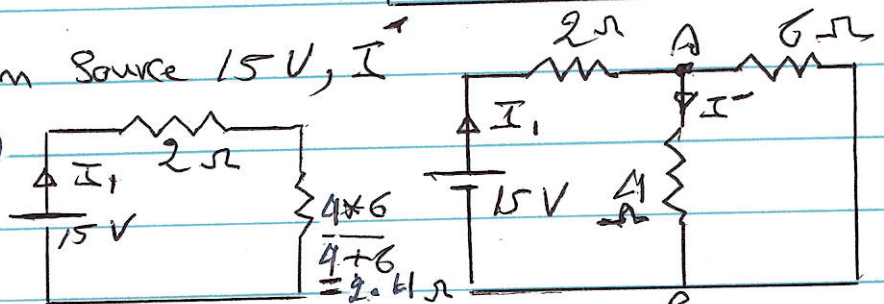

Ex (2.5)

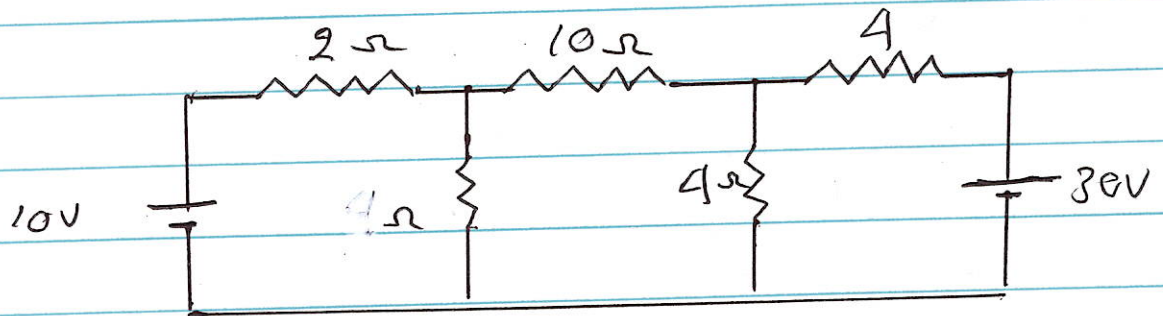
Using Thevenin's theorem, find current in $10\ \Omega$ resistance.



1- V_{th}

$$I_1 = \frac{10}{2+2} = 2.5 \text{ amp}$$
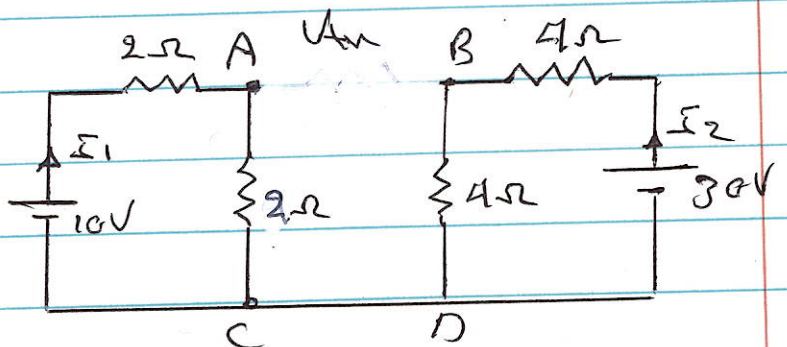
$$V_{AC} = 2.5 \times 2 = 5 \text{ Volt}$$



$$I_2 = \frac{30}{4+4} = 3.75 \text{ amp}$$


$$V_{BD} = 4 \times 3.75 = 15 \text{ Volt}$$

$$\therefore V_{AB} = V_{BD} - V_{AC} = 15 - 5 = 10 \text{ Volt}$$


$$V_{th} = V_{AB} = 10 \text{ Volt}$$

$$R_{th} = 2 \parallel 2 + 4 \parallel 4$$

$$= 1 + 2 = 3\ \Omega$$

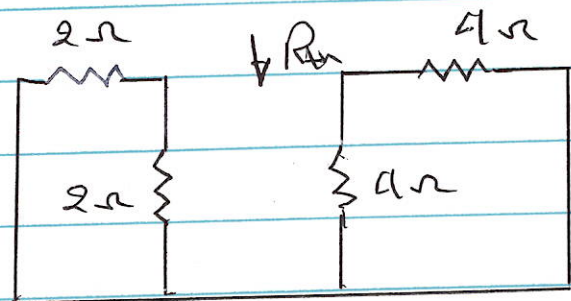

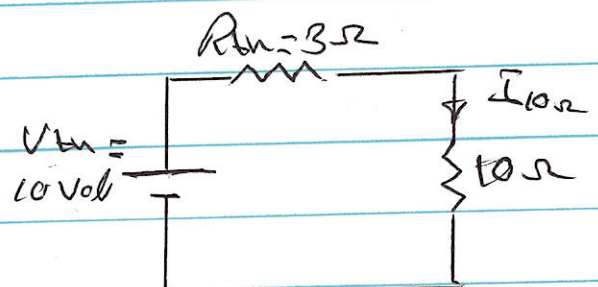
$$I_{10\Omega} = \frac{10}{3+10} = 0.7692 \text{ amp}$$



-16-

$$I^- = 3.409 \times \frac{6}{6+4} = 2.0454 \text{ amp. From A to B}$$

2. Current from source 20V, I^-

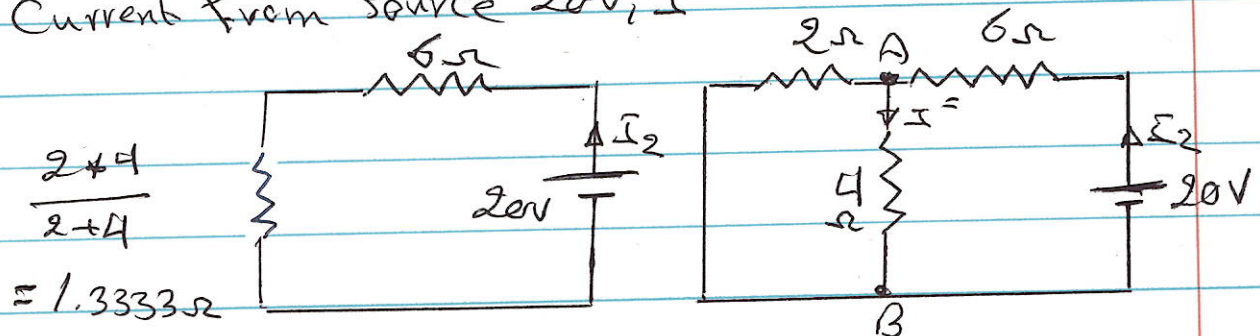


$$I_2 = \frac{20}{6+1.3333} = 2.7273 \text{ amp.}$$

$$I^- = I_2 \times \frac{2}{2+4} = 2.7273 \times \frac{2}{2+4} = 0.9091 \text{ amp. From A to B}$$

$$\begin{aligned} 3. \quad I_{4\Omega} &= I^- + I^- \\ &= 2.0454 + 0.9091 = 2.9545 \text{ amp} \\ &\text{From A to B} \end{aligned}$$





Ex(2.4)

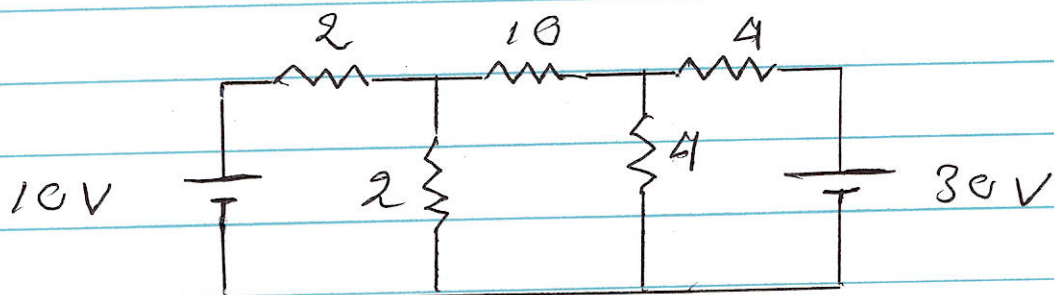Using superposition theorem, find current in 10Ω resistance.



- 17 -





1. Current From 10V source I^-

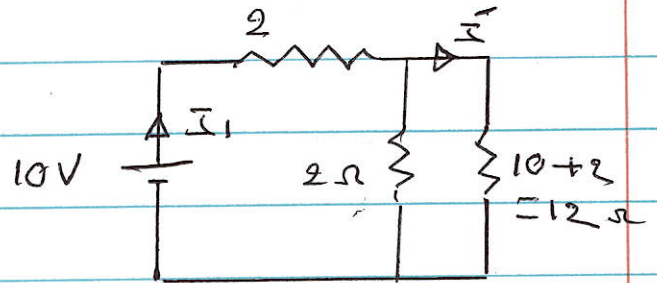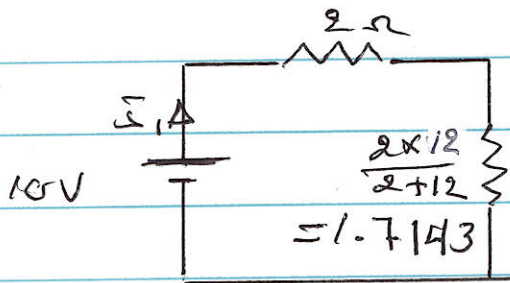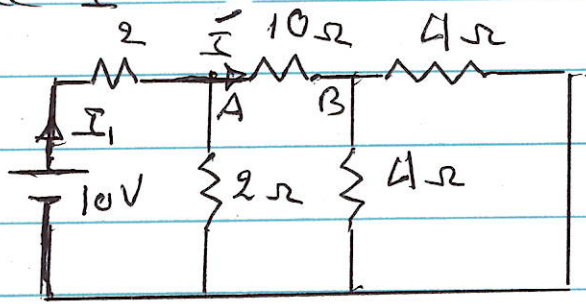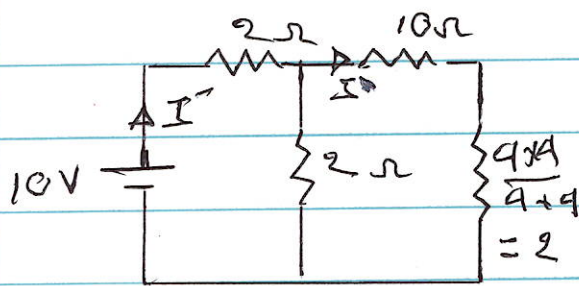

$$I_1 = \frac{10}{2 + 1.7143} = 2.6923$$

$$I^- = I_1 \times \frac{2}{2 + 12} = 0.3846 \text{ amp.}$$

2. Current From 20V source I^-

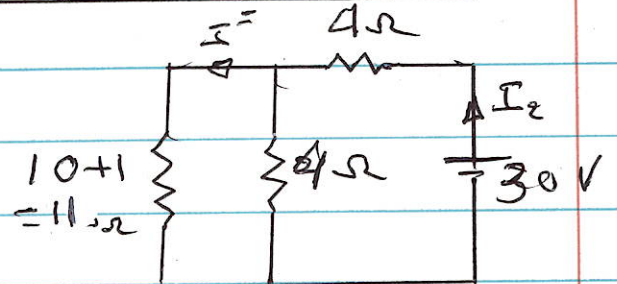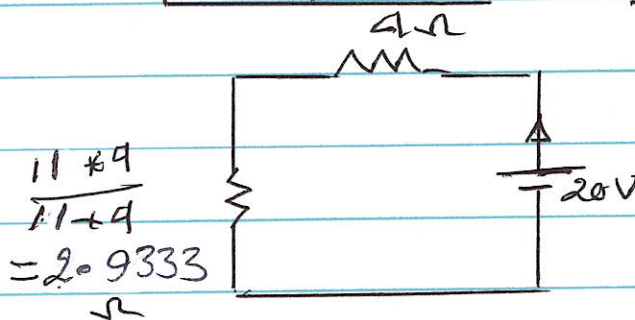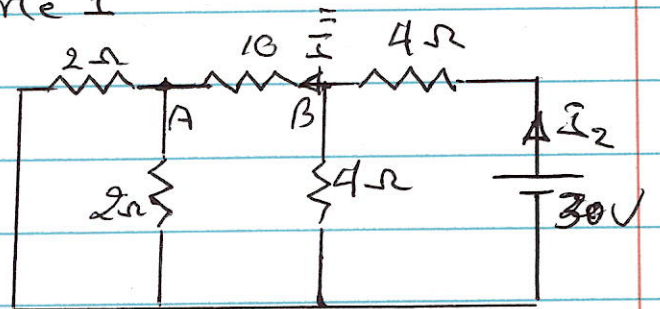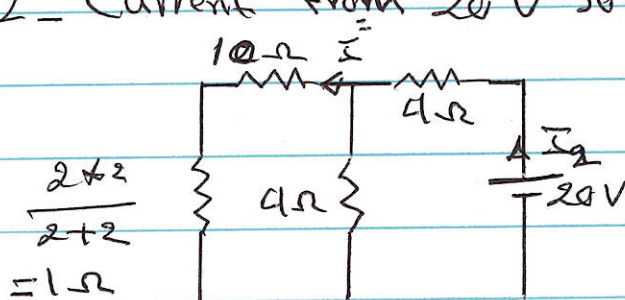

$$I_2 = \frac{20}{4 + 2.9333} = 4.3269 \text{ amp.}$$

$$I^- = I_2 \times \frac{4}{11 + 4} = 4.3269 \times \frac{4}{15} = 1.1538 \text{ amp From B to A}$$

-18-


$$3 - I_{10\Omega} = I^+ - I^-$$

$$= 1.1538 - 0.3846 = 0.7692 \text{ amp}$$


From B to A

2.4 - Thevenin's Theorem

To find current in R_3 I

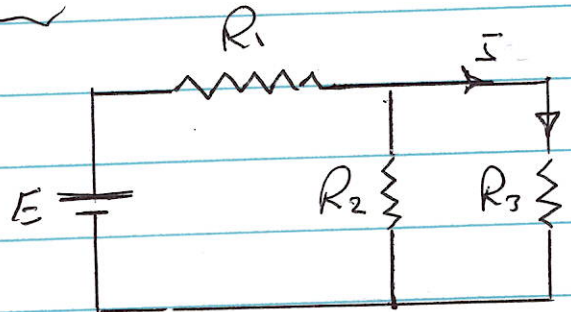


1 - V_{th}

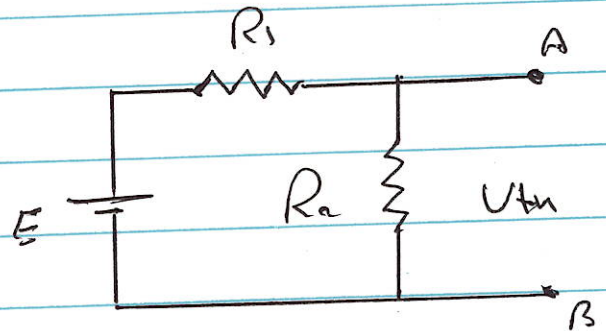


2 - R_{th}
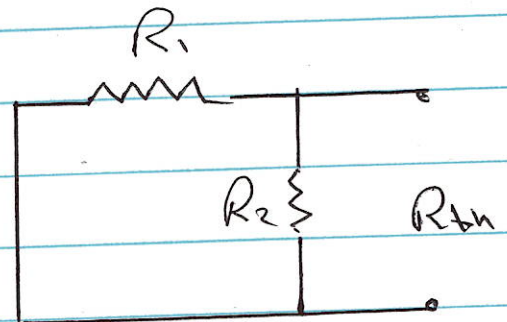
$$R_{th} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$




3 - Thevenin's Equivalent

$$I = \frac{V_{th}}{R_{th} + R_3}$$

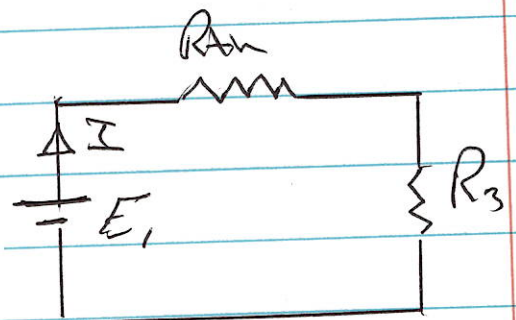

EX(2-5)

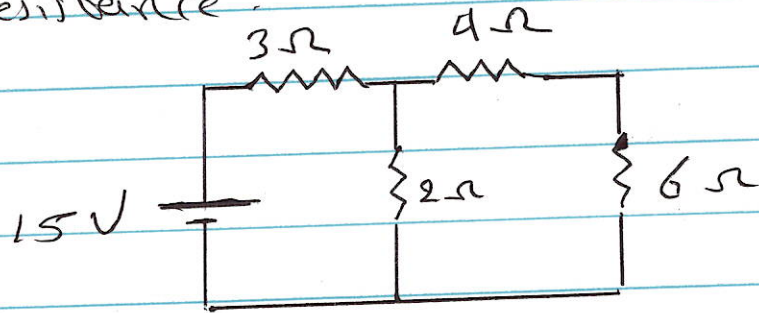
Using Thevenin's theorem, Find Current in $6\ \Omega$ resistance.



1- V_{th}

$$V_{th} = V_{AB} = V_{CD}$$
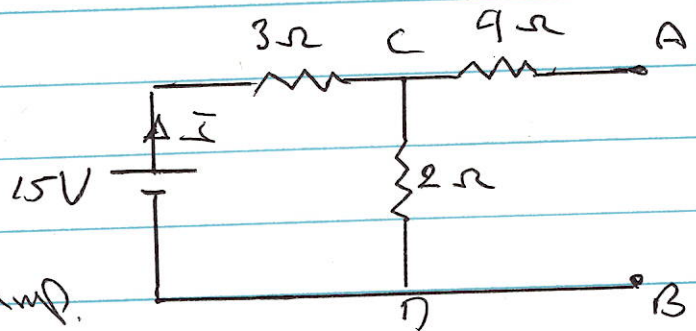
$$I = \frac{15}{3+2} = \frac{15}{5} = 3 \text{ amp.}$$




$$\therefore V_{CD} = 2 \times 3 = 6 \text{ volt}$$

$$\therefore V_{th} = 6 \text{ volt}$$

2- R_{th}

$$R_{th} = 4 + 3 \parallel 2$$

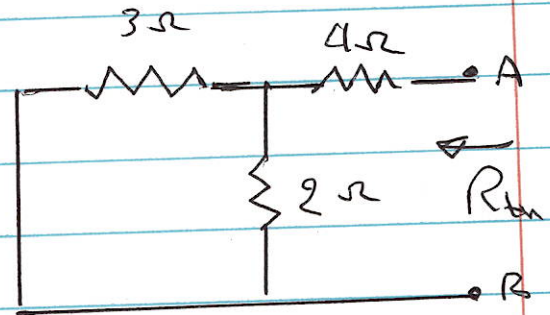
$$= 4 + \frac{3 \times 2}{3+2} = 5.2\ \Omega$$



$$I_{6\Omega} = \frac{V_{th}}{R_{th} + 6}$$

$$I_{6\Omega} = \frac{6}{6 + 5.2}$$


$$\frac{V_{th}}{= 6}$$

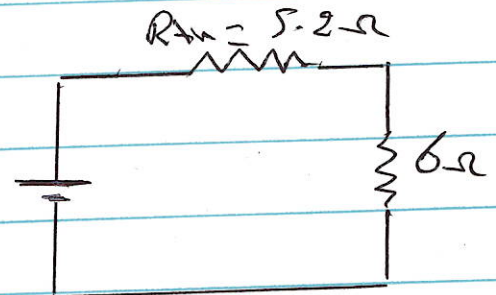

$$= 0.5357 \text{ amp.}$$




Current in $6\ \Omega$ resistance

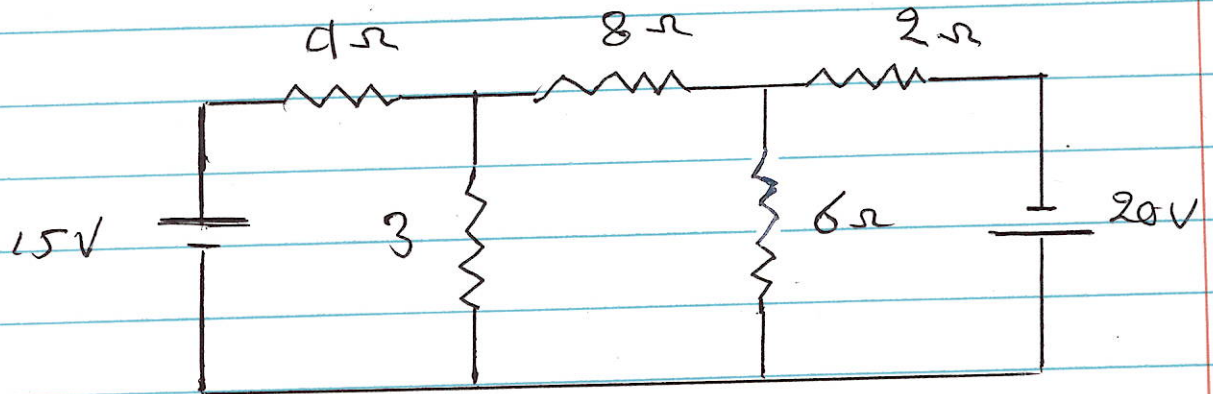Q-1 Using Thevenin's theorem find current in $8\ \Omega$ resistance.



Chapter - 3 - AC Fundamental

3.1 - AC Generation and WaveForms:

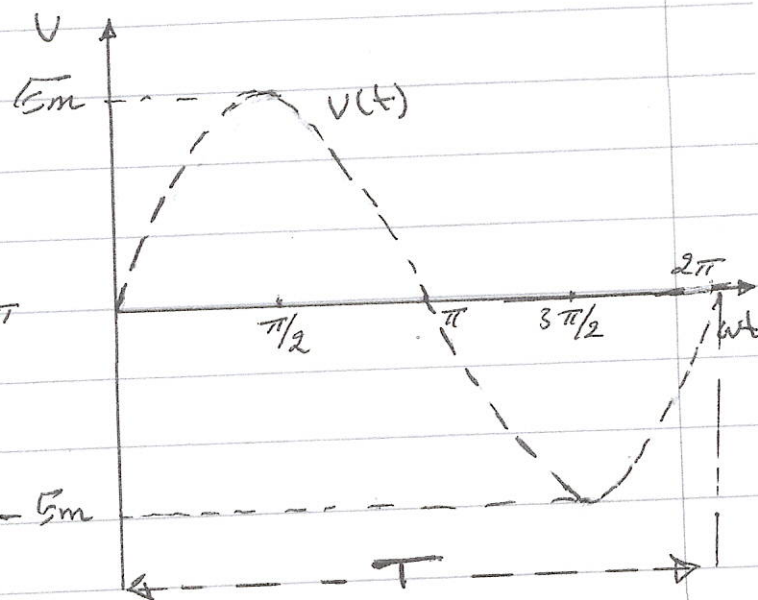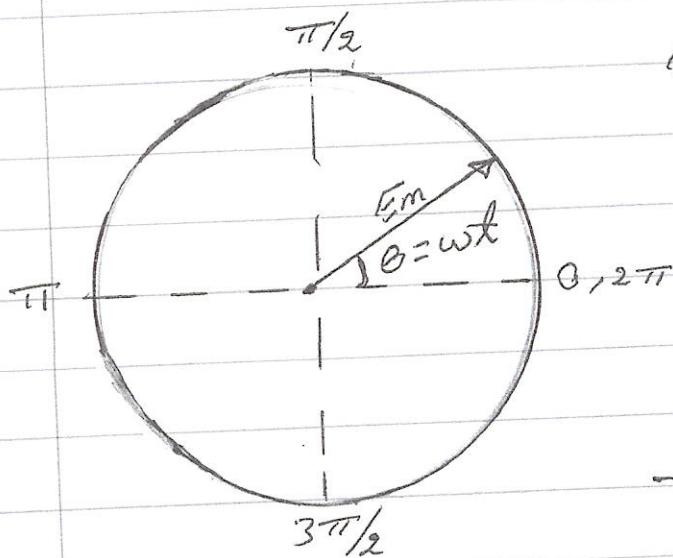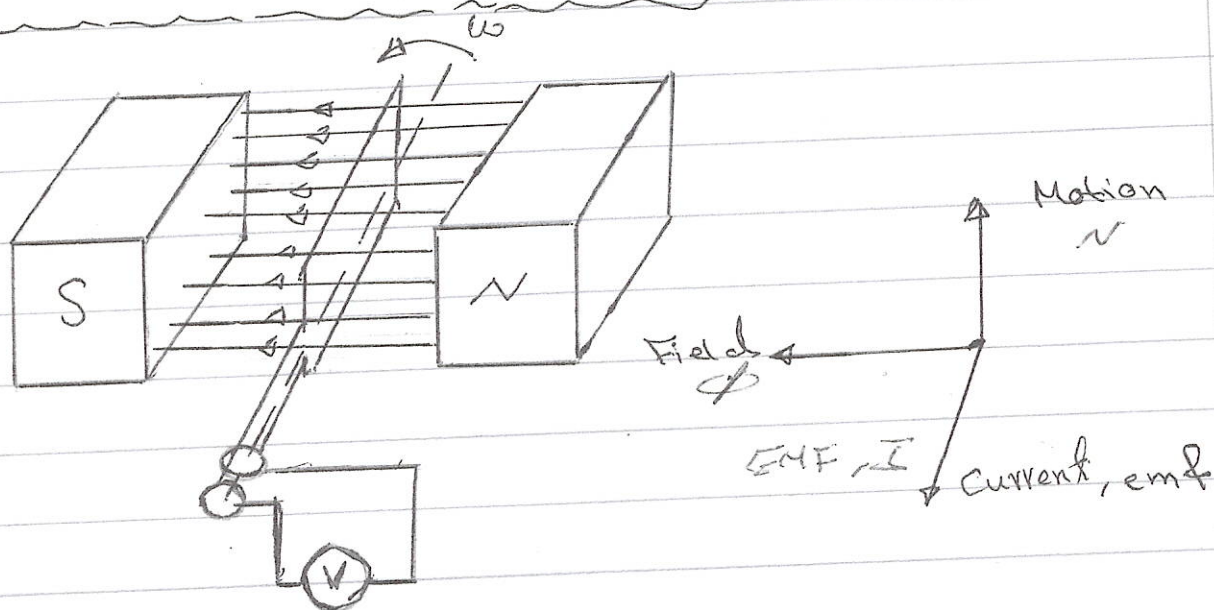

$$V(t) = E_m \sin \omega t \quad \text{--- (1)}$$

$$i(t) = I_m \sin(\omega t \pm \phi) \quad \text{--- (2)}$$

$V(t) + i(t)$: instantaneous values

ω : Angular speed rad/second

ϕ : Phase difference

$$\omega = 2\pi f$$



f : Frequency Hz (cycle/sec.)

$$f = \frac{1}{T} \quad \text{Hz} \quad \dots (3)$$

T : Time of one cycle (Sec.)

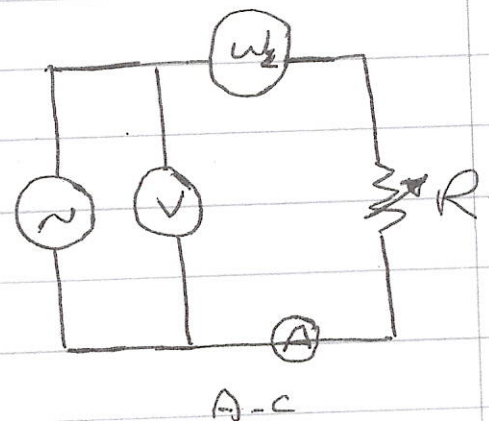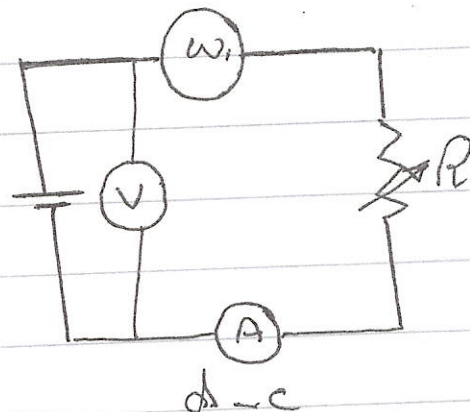3.2 - Root Mean Square (R.M.S.) Values

The (r.m.s.) value of an alternating current is given by that steady (d.c) current which when flowing through a given circuit for given time produces the same heat as produced by the alternating current when flowing through the same circuit for the same time.




$$W_1 = W_2$$

$$I_{r.m.s} = I_{d-c}$$

$$V_{r.m.s} = V_{d-c}$$

$$I_{r.m.s} = \frac{I_m}{\sqrt{2}} = 0.707 I_m \quad \dots (4)$$
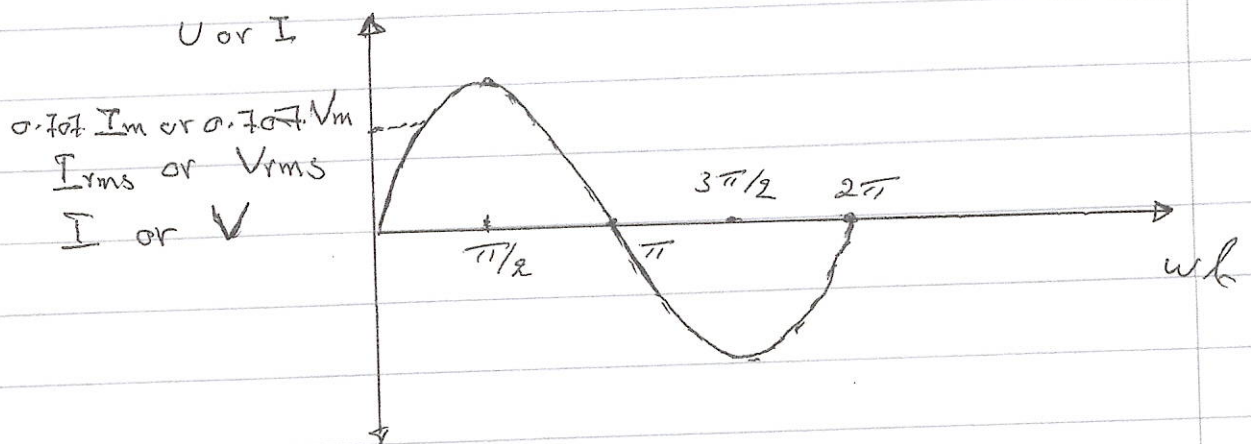
$$V_{r.m.s} = \frac{V_m}{\sqrt{2}} = 0.707 V_m \quad \dots (5)$$



Ex(3.1)

An alternating current varying sinusoidally with a frequency of 50 Hz has an RMS value of 20 amp. Write down the equation for the instantaneous value and find this value (a) 0.0025 second (b) 0.0125 second after first maximum value.

$$I = \frac{I_m}{\sqrt{2}} \quad \therefore I_m = \sqrt{2} \times 20 = 28.28 \text{ amp.}$$


$$\begin{aligned} \omega &= 2\pi f = 2\pi \times 50 = 100\pi \\ &= 100 \times 180^\circ = 18000^\circ \text{ degrees} \\ &= 100 \times 3.14 = 314 \text{ radians} \end{aligned}$$

(a)



$$\begin{aligned} i(t) &= I_m \sin \omega t \\ &= 28.28 \sin 18000 \times 0.0075 \\ &= 28.28 \sin 135^\circ \\ &= 20 \text{ amp.} \end{aligned}$$

$$T = \frac{1}{50} = 0.02 \text{ Sec}$$
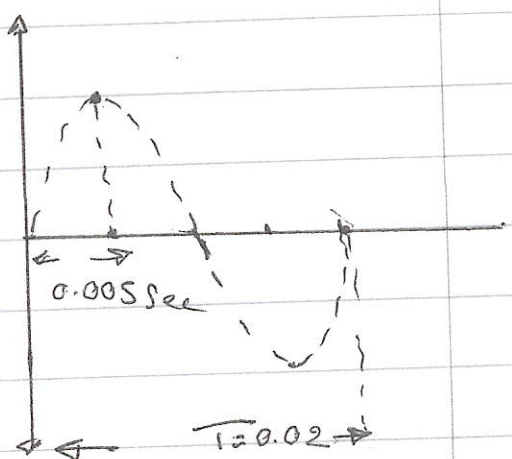
$$t = 0.005 + 0.0025 = 0.0075 \text{ Sec.}$$



3.3 - Pure Resistance

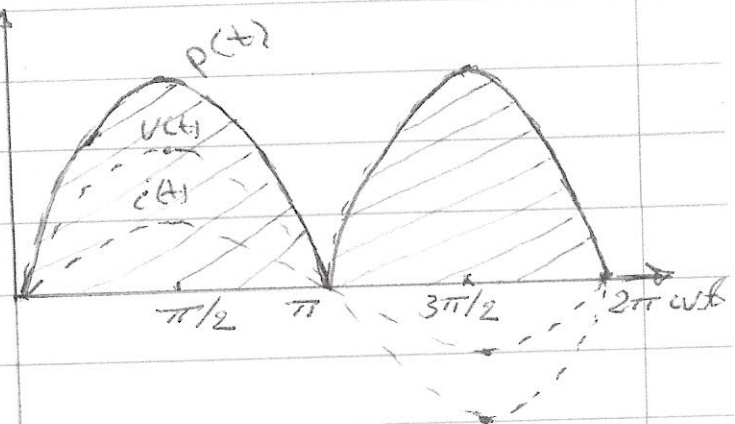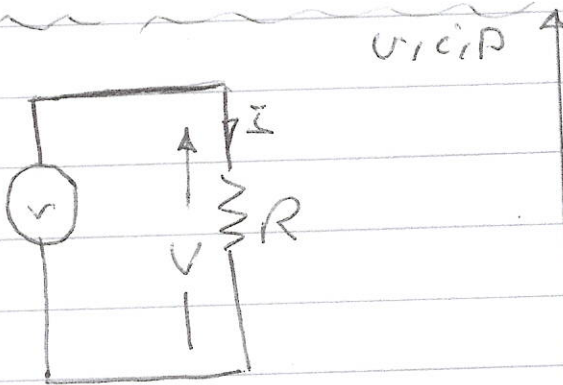

Waveform

$$V(t) = V_m \sin \omega t$$


$$i(t) = I_m \sin \omega t$$

$\phi = 0$ phase difference

$$P(t) = V(t) \cdot i(t)$$

$$P = VI \cos 0 = VI \quad \text{--- (6)}$$


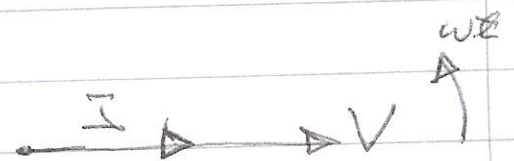
$$= I^2 R = \frac{V^2}{R} \quad \text{--- (7)}$$



Vector diagram

Phasor diagram

3.4 - Pure Inductance

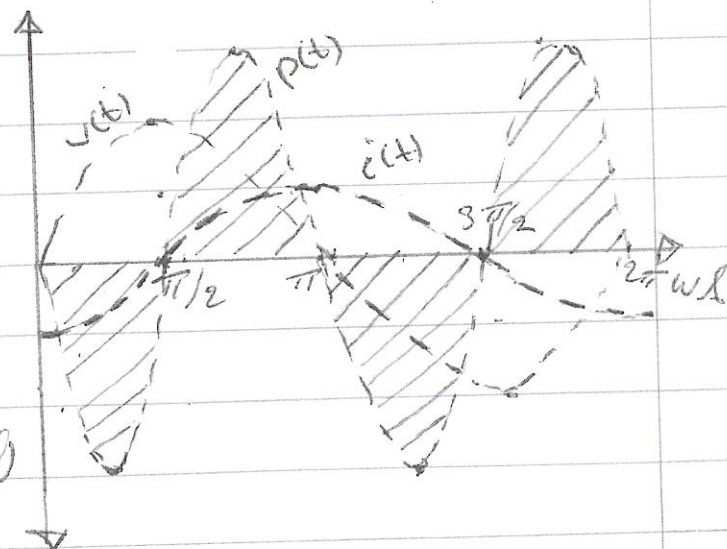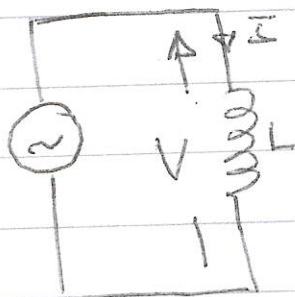

$$V(t) = V_m \sin \omega t$$

$$i(t) = I_m \sin(\omega t - \phi)$$

$\phi = 90^\circ$

$$P(t) = V(t) \cdot i'(t)$$

$$= 0 \quad \text{For one cycle}$$


$$P = VI \cos 90 = 0$$

$$X_L = 2\pi fL \quad \text{--- (8)}$$



L : inductance Henry (H)

X_L : inductive reactance Ω
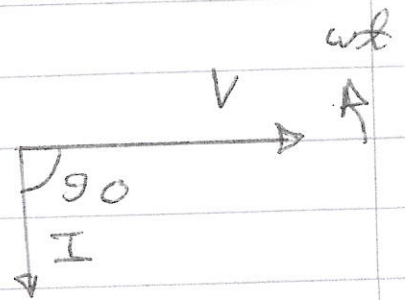
$$X_L = \frac{V}{I} \Omega \quad \text{--- (9)}$$



3.5 - Pure Capacitance

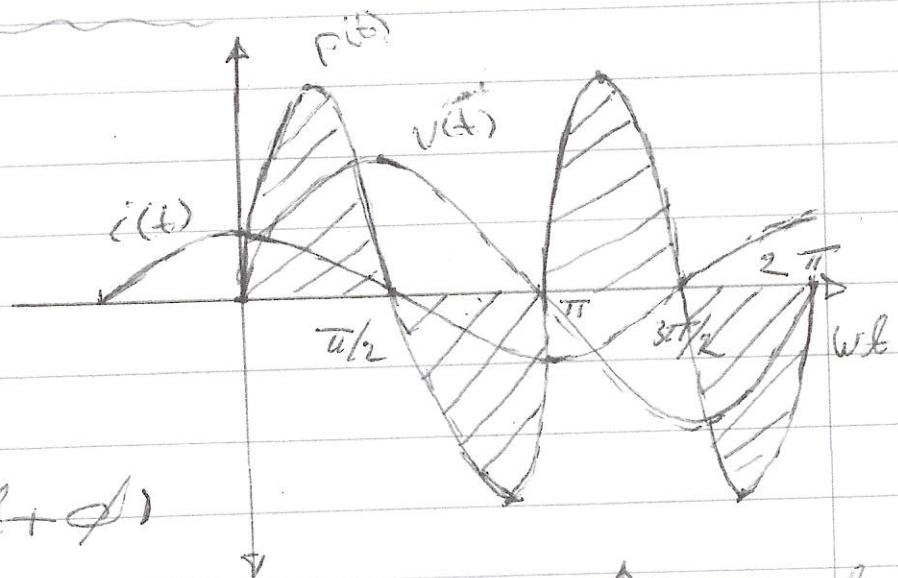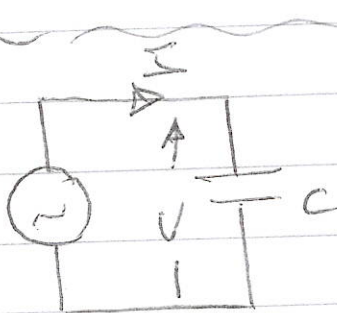


$$V(t) = V_m \sin \omega t$$

$$i(t) = I_m \sin(\omega t + \phi)$$

$$\phi = 90^\circ$$

$$P(t) = V(t) \cdot i'(t) = 0 \quad \text{For one cycle}$$
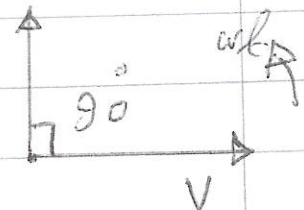
$$X_C = \frac{1}{2\pi fC} \Omega \quad \text{--- (10)}$$




C : Capacitance

X_C : Capacitive reactance Ω

$$P = VI \cos 90 = 0$$

$$X_C = \frac{V}{I} \quad \Omega \quad (11)$$

3.6 - Series RL Circuit

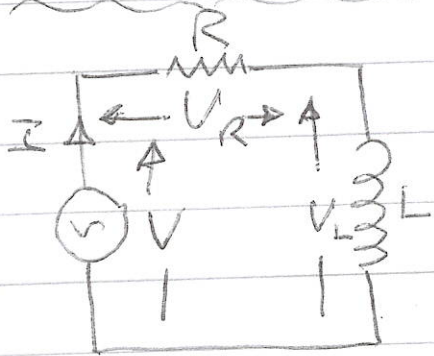

$$v(t) = V_m \sin \omega t$$

$$i(t) = I_m \sin(\omega t - \phi)$$

$$90^\circ > \phi > 0^\circ$$

$$P^+ > P^-$$

$$p(t) = v(t) \cdot i(t)$$

$$P = IV \cos \phi$$

ϕ is lagging




$$\phi = \tan^{-1} \frac{X_L}{R} \quad (12)$$

$$Z = \frac{V}{I} \quad \Omega \quad (13)$$

$$Z = \sqrt{R^2 + X_L^2} = |Z| \angle \phi \quad \Omega \quad (14)$$


$$\cos \phi : \text{Power Factor} \quad (15)$$

$$V = \sqrt{V_R^2 + V_L^2} \quad (16)$$

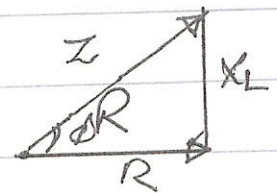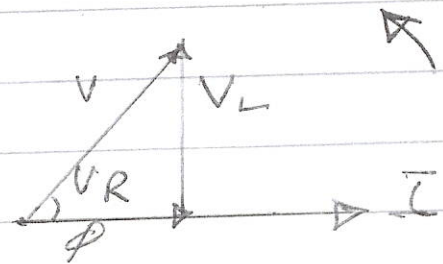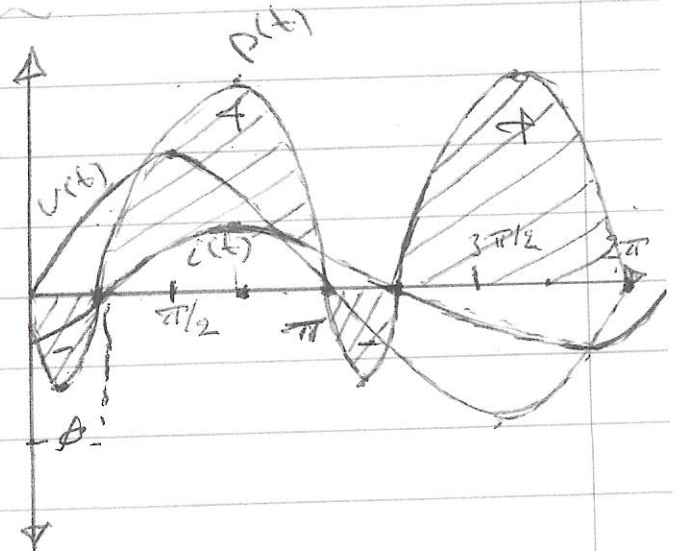

Ex(3.2): The potential difference measured across a coil is 4.5 V, when it carries a direct current of 9 amp. The same coil when carries an alternating current of 9 amp. at 25 Hz, the potential difference is 24 V. Find the current, the power factor when its supplied by 50 V, 50 Hz supply. Skin effect is 1.1 at 25 Hz and 1.2 at 50 Hz.
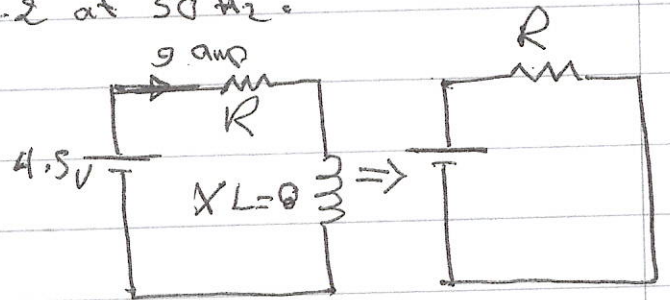
$$R = \frac{V_{dc}}{I_{dc}} = \frac{4.5}{9} = 0.5 \Omega$$



$$\text{at } 25 \text{ Hz } R = 1.1 \times R_{dc} \\ = 1.1 \times 0.5 = 0.55 \Omega$$

$$\text{at } 50 \text{ Hz } R = 1.2 \times R_{dc} = 1.2 \times 0.5 = 0.6 \Omega$$

$$\text{at } 25 \text{ Hz } V = 24 \text{ V}, I = 9 \text{ amp.}$$

$$\therefore Z = \frac{V}{I} = \frac{24}{9} = 2.666 \Omega$$

$$X_L = \sqrt{Z^2 - R^2} = \sqrt{(2.666)^2 - (0.55)^2} = 2.608$$

$$X_L = 2\pi fL \quad 2.608 = 2 \times 3.14 \times 25 L$$

$$L = 0.0166 \text{ H}$$

$$\text{at } 50 \text{ Hz } V = 50 \text{ Volt}$$

$$X_L = 2\pi fL = 2 \times 3.14 \times 50 \times 0.0166 = 5.2124 \Omega$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{(0.6)^2 + 5.2124^2} = 5.247 \Omega$$

$$I = \frac{V}{Z} = 50 / 5.247 = 9.529 \text{ amp}$$

$$P.F. = \cos \phi$$

$$\phi = \tan^{-1} \frac{X_L}{R} = \tan^{-1} \left(\frac{5.2124}{0.6} \right) =$$

$$\phi = 83.43^\circ$$


$$P = IV \cos \phi$$

$$= 9.529 \times 50 \times \cos(83.43) = 54.514 \text{ watt}$$

$$\text{or } P = I^2 R = (9.529)^2 \times 0.6 = 54.481 \text{ watt}$$

$$P.F. = \cos \phi = \cos(83.43) = 0.1144$$

3.7 - Series R-C circuit

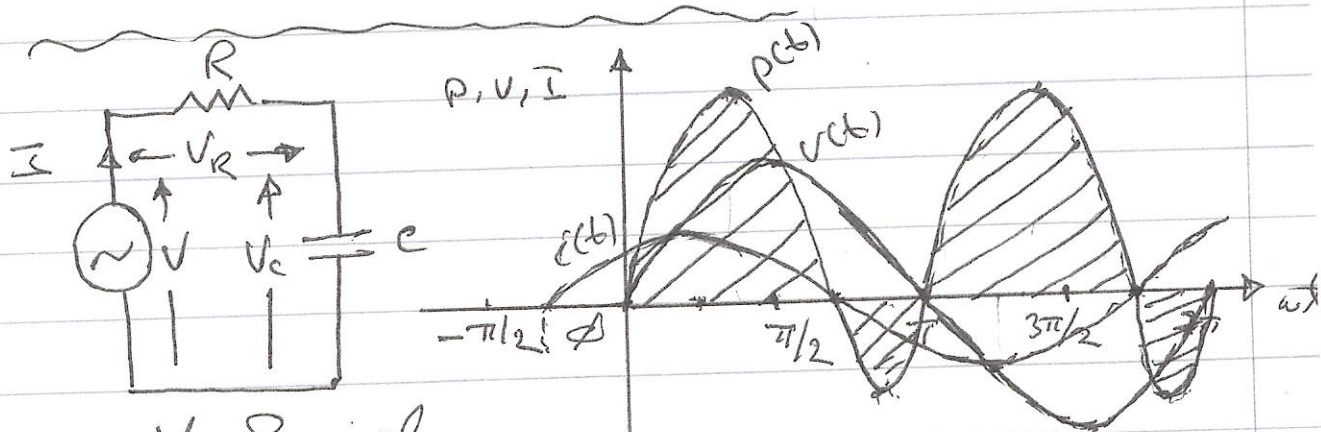

$$v(t) = V_m \sin \omega t$$

$$i(t) = I_m \sin(\omega t + \phi)$$

$$90^\circ > \phi > 0$$



$$P^+ > P^-$$

$$p(t) = v(t) \cdot i(t)$$

ϕ is leading

$$\phi = \tan^{-1} \left(-\frac{X_C}{R} \right) \quad (16)$$

$$V = \sqrt{V_R^2 + V_C^2} \quad (18)$$

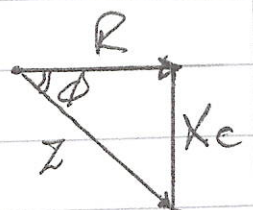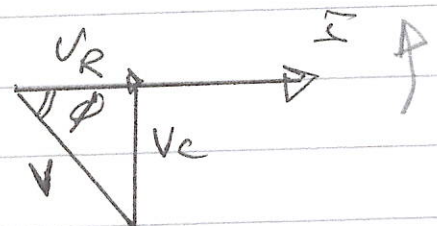

$$Z = \frac{V}{I}$$

$$Z = \sqrt{R^2 + X_C^2} = |Z| \angle -\phi \quad \Omega \quad \dots (17)$$

$$X_C = \frac{1}{2\pi fC} \quad \Omega \quad \dots (18)$$

C: Capacitance Farad (F)

Ex 3.3:

A pure resistance of 50 Ohms with a pure capacitance of 100 microFarad (μF). The series combination is connected across 100 V, 50-Hz. Find (a) the impedance (b) current (c) power factor (d) phase angle (e) voltage across resistance (f) voltage across capacitor. Draw the vector diagram.

Solution:

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2 \times 3.14 \times 50 \times 100 \times 10^{-6}} = 31.19 \Omega$$

$$R = 50 \Omega$$

$$(a) \quad Z = \sqrt{R^2 + X_C^2} = \sqrt{50^2 + 31.19^2} = 58.93 \Omega$$

$$(b) \quad |I| = \frac{V}{|Z|} = \frac{100}{58.9} = 1.7 \text{ amp.}$$

$$(c) \quad \phi = \tan^{-1} \frac{X_C}{R} = \tan^{-1} \left(\frac{31.19}{50} \right) = 31.956$$


$$P.F. = \cos \phi = \cos(31.956) = 0.848 \text{ leading}$$

$$(d) \quad \phi = 31.956^\circ \text{ leading phase shift (angle)}$$


$$(e) \quad |V_R| = IR = 85 \text{ volt}$$

$$(f) \quad |V_C| = I X_C = 1.7 \times 31.19 = 53.023$$




(Phasor) Vector diagram

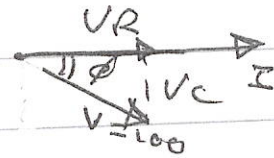

3.8 - Series R-L-C circuit

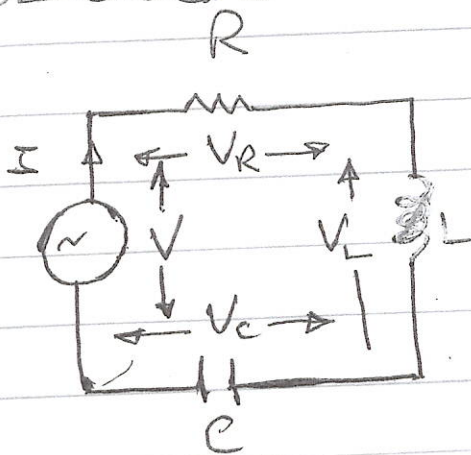

$X_L < X_C$

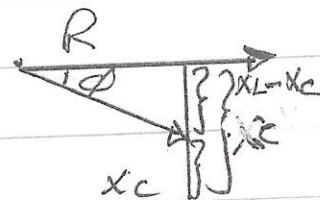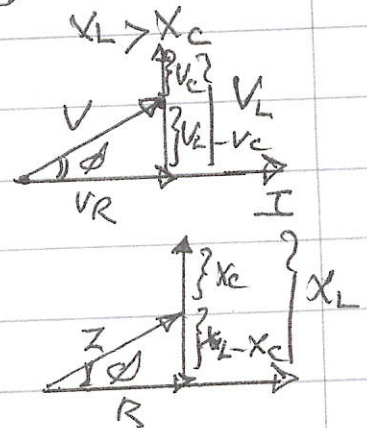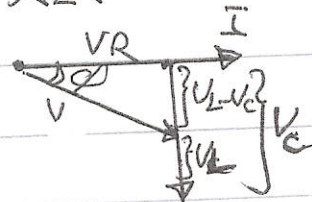

$$V = \sqrt{V_R^2 + (V_L - V_C)^2} \quad \text{— volt — (19)}$$


$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + X^2} \quad \text{— (20)}$$

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right) = \tan^{-1} \left(\frac{X}{R} \right) \quad \text{— (21)}$$

$$X = X_L - X_C$$

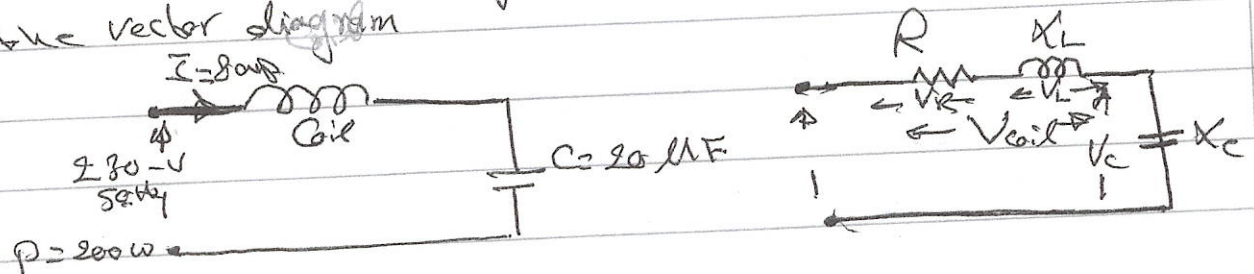Q.4) Ex (P.4):

A coil is in series with 20 μ F capacitor across a 230-V, 50-Hz supply. The current taken by the circuit is 8 amp. and the power consumed is 200W. calculate the voltage across the coil and draw the vector diagram



$$P = I^2 R \quad 200 = 8^2 R \quad R = \frac{200}{64} = 3.125 \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 50 \times 20 \times 10^{-6}} = 159.23 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} \quad \text{or} \quad Z^2 = R^2 + (X_L - X_C)^2$$

$$Z = \frac{V}{I} = \frac{230}{8} = 28.75 \Omega$$

$$(28.75)^2 = (3.125)^2 + (X_L - 159.23)^2$$

$$(X_L - 159.23)^2 = 816.79$$

$$X_L - 159.23 = 28.58 \quad \therefore X_L = 187.81 \Omega$$

$$Z_{\text{coil}} = \sqrt{R^2 + X_L^2} = \sqrt{3.125^2 + 187.81^2} = 187.83 \Omega$$

$$V_{\text{coil}} = I Z_{\text{coil}} = 8 \times 187.83 = 1502.64 \text{ volt}$$


$$V_L = I X_L = 8 \times 187.81 = 1502.48 \text{ volt}$$

$$V_C = I X_C = 1273.84 = 8 \times 159.23$$

$$V_R = I R = 8 \times 3.125 = 25 \text{ volt}$$

-35-

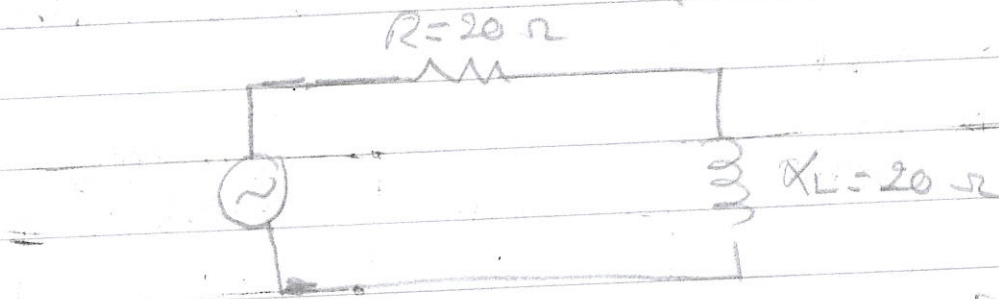- Q1 - For the circuit shown in Fig. if the supply is $220\text{V}, 50\text{Hz}$, find (a) the voltage across each element, (b) power consumed and (c) draw phasor diagram.




- Q2 - For the circuit shown in Fig, find (a) voltage across each element (b) power consumed (c) draw phasor diagram and waveform.

Supply $200\text{V}, 50\text{Hz}$

$R = 50\ \Omega$

$X_C = 80\ \Omega$

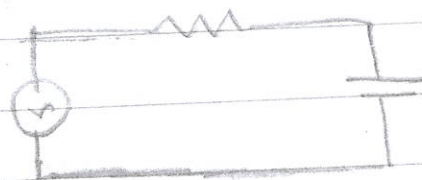

- Q3 - For the circuit shown in Fig, find (a) voltage across each element (b) power consumed (c) draw phasor diagram.

